A FEW WAYS TO ORGANIZE THE TRAFFIC LIGHT LOGIC

	Main Street			Side Street		
	Red	Yellow	Green	Red	Yellow	Green
	Y0	Y1	Y2	Y3	Y4	Y5
C0	X			X		
T0			X	X		
T1		X		X		
T2	X			X		
T3	X					X
T4	X				X	
T5	**RESET**					

	TURNS ON			TURNS OFF
C0	Y0	Y3	T0	
T0	Y2	T1		Y0
T1	Y1	T2		Y2
T2	Y0	T3		Y1
T3	Y5	T4		Y3
T4	Y4	T5		Y5
T5	RESETS T0			

RTUNSTALL 19 14 2020

A FEW WAYS TO ORGANIZE THE TRAFFIC LIGHT LOGIC

WHEN THE ELEMENT BELOW IS ENERGIZED	THESE ACTIONS BELOW RESULT		
COIL 0	TURNS ON OUTPUT Y0	TURNS ON OUTPUT Y3	STARTS TIMER 0
TIMER 0	TURNS OFF OUTPUT Y0	TURNS ON OUTPUT Y2	STARTS TIMER 1
TIMER 1	TURNS OFF OUTPUT Y2	TURNS ON OUTPUT Y1	STARTS TIMER 2
TIMER 2	TURNS OFF OUTPUT Y1	TURNS ON OUTPUT Y0	STARTS TIMER 3
TIMER 3	TURNS OFF OUTPUT Y3	TURNS ON OUTPUT Y5	STARTS TIMER 4
TIMER 4	TURNS OFF OUTPUT Y5	TURNS ON OUTPUT Y4	STARTS TIMER 5
TIMER 5	RESETS TIMER 0		

MAIN	Red Y0	X			X	X	X	RESET
	Yellow Y1			X				
	Green Y2		X					
SIDE	Red Y3	X	X	X	X			
	Yellow Y4						X	
	Green Y5					X		
		CO	T0	T1	T2	T3	T4	T5

RTUNSTALL 19 14 2020